



DAY-13


#100DAYSRTL

“Aim”:- To Design the CMOS inverter using Verilog

“Verilog Code”:-

```
module cmos_inverter(  
    input in,  
    output out  
);  
    supply0 gnd;  
    supply1 vdd;  
    //pmos(drain,source,gate);  
    pmos (out, vdd, in);  
    //nmos(drain,source,gate);  
    nmos (out, gnd, in);  
endmodule
```

“Schematics”:-

 

“Waveforms”:-

