



## DAY-32


### #100DAYSRTL

**“Aim”:-** To Design Universal Shift register which performs linear circular left and right shift operations


### “Design Code”:-

```
module usr_shift_reg_b1(input clk,rst,lrbar,lcbar,input [3:0]i,output reg [3:0]y);
always @ (posedge clk)begin
if(rst) y<=i;
else
begin
case({lrbar,lcbar})
2'b00:begin y<={y[0],y[3:1]}; end
2'b01: begin y<={1'b0,y[3:1]}; end
2'b10: begin y<={y[2:0],y[3]}; end
2'b11: begin y<={y[2:0],1'b0}; end
default: begin end
endcase
end
end
endmodule
```

### “Schematics”:-

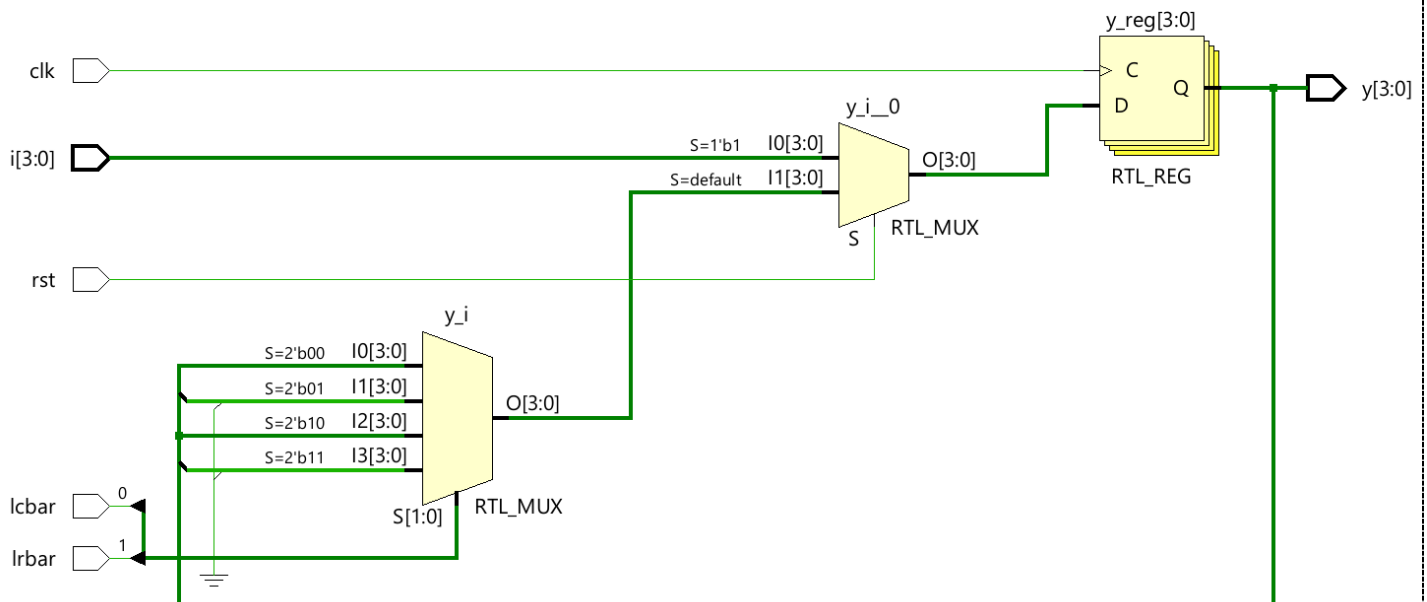

# “Waveforms”:-

 

## Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

**Total On-Chip Power:** 2.003 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 28.8°C  
Thermal Margin: 56.2°C (29.7 W)  
Effective  $\theta_{JA}$ : 1.9°C/W  
Power supplied to off-chip devices: 0 W  
Confidence level: Low  
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

## On-Chip Power

