


# DAY-21 #100DAYSRTL

"Aim":-To Design a MUX that acts as an Asynchronous PISO

"Design Code":-

```
module Mux #(parameter N = 32, M = 5) ( //M=log2(M)
    input [N-1:0] A, //Parallel Data as input
    input [M-1:0] S,
    output reg Y // Serial Data as output
);
always @(*) begin
for(int i=0;i<N;i++) begin
case (S)
i:Y=A[i];
endcase
end
end
end
endmodule</pre>
```

### "Schematics":-

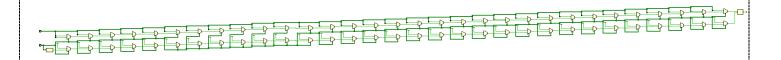

## "Waveforms":-

Name	Value	0.000 ns		50.000 ns		100	000 ns		150	000 n	s , ,	21	000,000	ns		25	,000	ns		300.0	00
> MA[31:0]	00000000	00000000000000001001101101000																			
> <b>V</b> S[4:0]	11111	()()()	()	()()	χχ	X>	(··)(··)	()()	(···)		77	/ -	.)()	()	χ.	· ./	χ	XX	X	X X -	
<b>™</b> Y	0																				

#### "Console":-

A=000000000000000000010011011011000, S=00000, Y=0 A=000000000000000000010011011011000,S=00001,Y=0 A=000000000000000000010011011011000, S=00010, Y=0 A=000000000000000000010011011011000, S=00011, Y=1 A=000000000000000000010011011011000, S=00100, Y=1 A=000000000000000000010011011011000, S=00101, Y=0 A=000000000000000000010011011011000, S=00110, Y=1 A=000000000000000000010011011011000, S=00111, Y=1 A=000000000000000000010011011011000, S=01000, Y=0 A=000000000000000000010011011011000, S=01001, Y=1 A=000000000000000000010011011011000,S=01010,Y=1 A=000000000000000000010011011011000, S=01011, Y=0 A=000000000000000000010011011011000,S=01100,Y=0 A=000000000000000000010011011011000,S=01101,Y=1 A=000000000000000000010011011011000, S=01110, Y=0 A=000000000000000000010011011011000, S=01111, Y=0 A=000000000000000000010011011011000,S=10000,Y=0 A=000000000000000000010011011011000, S=10001, Y=0 A=000000000000000000010011011011000, S=10010, Y=0 A=000000000000000000010011011011000, S=10011, Y=0 A=000000000000000000010011011011000, S=10100, Y=0 A=000000000000000000010011011011000, S=10101, Y=0 A=000000000000000000010011011011000, S=10110, Y=0 A=000000000000000000010011011011000, S=10111, Y=0 A=000000000000000000010011011011000, S=11000, Y=0 A=000000000000000000010011011011000, S=11001, Y=0 A=000000000000000000010011011011000, S=11010, Y=0 A=000000000000000000010011011011000, S=11011, Y=0 A=000000000000000000010011011011000, S=11100, Y=0 A=000000000000000000010011011011000, S=11101, Y=0 A=000000000000000000010011011011000, S=11110, Y=0 A=000000000000000000010011011011000, S=11111, Y=0 Completed

#### Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.441 W

Design Power Budget: Not Specified

Power Budget Margin: N/A
Junction Temperature: 25.8°C

Thermal Margin: 59.2°C (31.2 W)

Effective θJA: 1.9°C/W

Power supplied to off-chip devices: 0 W
Confidence level:

Launch Power Constraint Advisor to find and fix

invalid switching activity

