



## DAY-19


### #100DAYSRTL

**“Aim”:-** To Design the Binary Digit Counter Which Counts the occurrence of ones and zeros.

### “Design Code”:-

```
module BinaryDigitCounter(
    input [3:0] Data_in,
    output reg [1:0] CountOfOnes,
    output reg [1:0] CountOfZeros,
    output reg [1:0] CountOfXandZ
);
    always @(*) begin
        CountOfOnes = 0;
        CountOfZeros = 0;
        CountOfXandZ=0;
        for (int i = 0; i < 4; i = i + 1) begin
            if (Data_in[i]) // To count the occurrence of ones
                CountOfOnes = CountOfOnes + 1;
            else if (~Data_in[i]) // To count the occurrence of Zeros
                CountOfZeros = CountOfZeros + 1;
            else if (Data_in[i]==1'bX) // To count the occurrence of Unknowns
                CountOfXandZ=CountOfXandZ+1;
        end
    end
endmodule
```

### “Schematics”:-

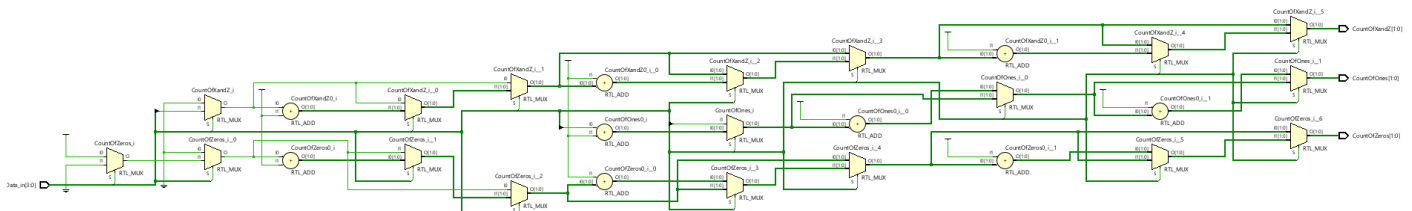

### “Waveforms”:-

