


DAY-38 #100DAYSRTL

"Aim":-To Design a Universal Counter (Down & Up)


"Design Code":-

```
module Counter(input rst,clk,en,udbar,ld,input [3:0] ld_val,output reg [3:0] cnt);
|always @(posedge clk)
begin
if (rst) cnt<=0;
else
begin
if(en) begin
if (ld) cnt<=ld val;
else begin
if (udbar) cnt<=cnt+1;
else cnt<=cnt-1;
end
end!
end
end
endmodule
```


"Waveforms":-

 

"Elaborated Design":-

 

"Implemented Design":-

 

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 2.816 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 30.3°C

Thermal Margin: 54.7°C (28.8 W)

Effective ϑJA : 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

Launch Power Constraint Advisor to find and fix

invalid switching activity

