



DAY-37


#100DAYSRTL

“Aim”:-To Design a Synchronous series counter


“Design Code”:-

```
module SSC(input clk,rst,output [2:0] count);  
  wire [2:0] q;  
  t_ff T0(1'b1,rst,clk,q[0]);  
  t_ff T1(q[0],rst,clk,q[1]);  
  t_ff T3((q[1]&q[0]),rst,clk,q[2]);  
  assign count=q;  
endmodule  
  
module t_ff(input T,rst,clk,output reg q);  
  always @(posedge clk) begin  
    if(rst) q<=1'b0;  
    else begin  
      case (T)  
        1'b0:q<=q;  
        1'b1:q<=~q;  
        default : begin ; end  
      endcase  
    end  
  end  
endmodule
```

“Waveforms”:-

 

“Schematics”:-

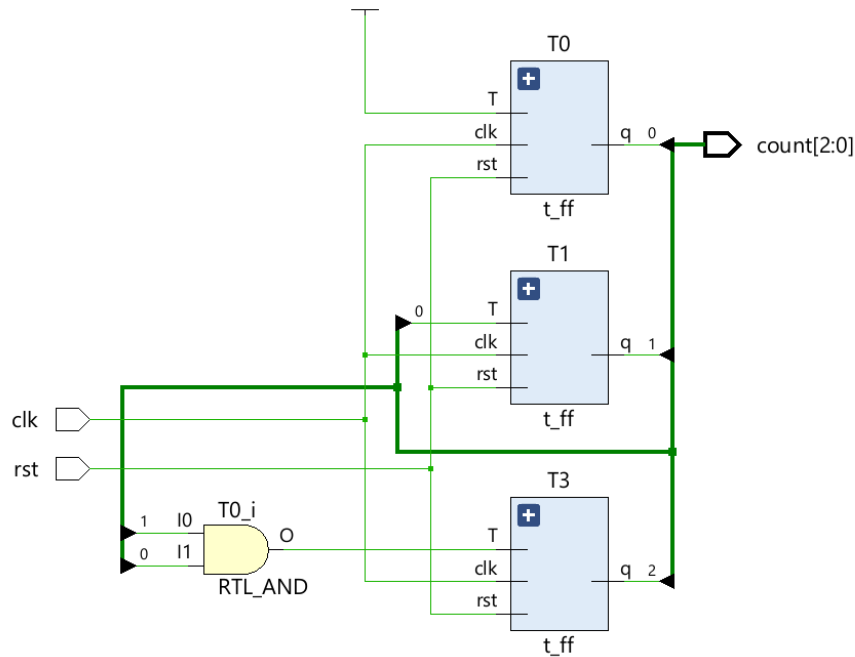

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 1.581 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 28.0°C
Thermal Margin: 57.0°C (30.1 W)
Effective θ_{JA} : 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

